

# Lab 5 - Counter

## CS1050 Computer Organization and Digital Design

Name : **Dissanayake D.M.A.K.**

Index No. : **220135N**

Group : **44**

### Lab Task:

Designing a 3 bit up / down counter using D flip-flops and slow down clock. First we completed the truth table and got expressions for D0, D1, D2. Then we created D flip flop and slow down clock. By using these D flip flops and slow down clock we created the counter.

### Introduction

We initiate the lab by examining D flip-flop excitation tables and streamlining equations using Karnaugh Maps. Following this, we progress to VHDL modeling of D flip-flops. Additionally, we establish a slowing counter model to effectively regulate clock frequencies, ensuring optimal visibility.

The central objectives of the lab involve constructing the 3-bit counter circuit, incorporating the derived Boolean expressions, and integrating the slowing counter to manage clock pulses efficiently. Rigorous simulation is employed to validate the counter's performance and functionality before advancing to hardware verification using the BASYS 3 board.

### Excitation Table of D Flip-Flop

$Q_t$	$Q_{t+1}$	D
0	0	0
0	1	1
1	0	0
1	1	1

### State Table of Counter

Q <sub>t</sub>			Button	Q <sub>t+1</sub>			D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>		Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>			
0	0	0	0	0	0	1	0	0	1
0	0	0	1	1	0	0	1	0	0
0	0	1	0	0	1	1	0	1	1
0	0	1	1	0	0	0	0	0	0
0	1	0	0	X	X	X	X	X	X
0	1	0	1	X	X	X	X	X	X
0	1	1	0	1	1	1	1	1	1
0	1	1	1	0	0	1	0	0	1
1	0	0	0	0	0	0	0	0	0
1	0	0	1	1	1	0	1	1	0
1	0	1	0	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X
1	1	0	0	1	0	0	1	0	0
1	1	0	1	1	1	1	1	1	1
1	1	1	0	1	1	0	1	1	0
1	1	1	1	0	1	1	0	1	1

### Karnaugh Maps for three Inputs

We can derive the boolean expressions for the inputs D<sub>2</sub>, D<sub>1</sub> and D<sub>0</sub> based Q<sub>t</sub> and B.

**For D<sub>0</sub>**

Q <sub>2</sub> Q <sub>1</sub>	00	01	11	10
Q <sub>0</sub> B				
00	1	X	0	0
01	0	X	1	0
11	0	1	1	X
10	1	1	0	X

$$D_0 = Q_1 \cdot B + Q'_2 \cdot B'$$

For D1

$Q_2Q_1$ $Q_0B$	00	01	11	10
00	0	X	0	0
01	0	X	1	1
11	0	0	1	X
10	1	1	1	X

$$D_1 = Q_2.B + Q_0.B'$$

For D2

$Q_2Q_1$ $Q_0B$	00	01	11	10
00	0	X	1	0
01	1	X	1	1
11	0	0	0	X
10	0	1	1	X

$$D_2 = Q'_0.B + Q_1.B'$$

# 1)D Flip Flop

## Design Source File

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity D_FF is
    Port ( D : in STD_LOGIC;
          Res : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC;
          Qbar : out STD_LOGIC);
end D_FF;


architecture Behavioral of D_FF is

begin
    process (Clk)begin

        if(rising_edge(Clk))
        then
            if Res = '1' then
                Q <= '0';
                Qbar <= '1';
            else
                Q <= D;
                Qbar <= not D;
            end if;
        end if;
    end process;

end Behavioral;
```

## Elaborated design schematic.

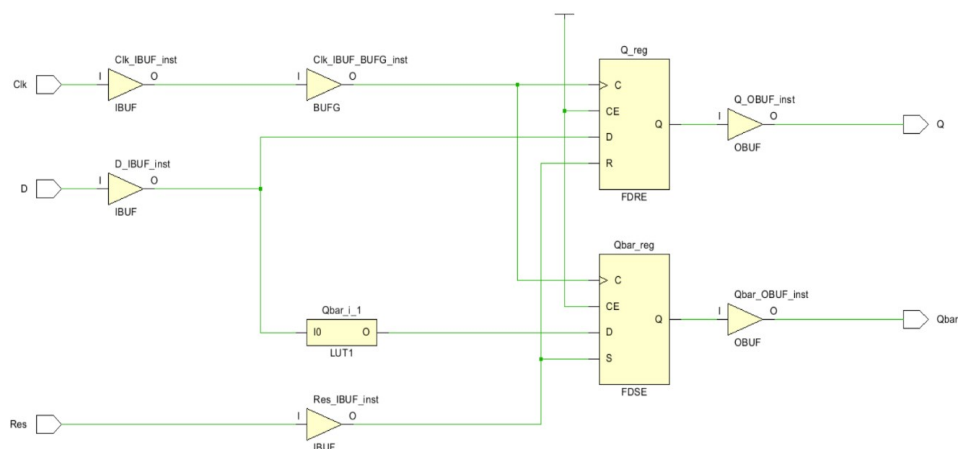

### Simulation source file

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity D_FF_Sim is
-- Port ( );
end D_FF_Sim;

architecture Behavioral of D_FF_Sim is

Component D_FF
    Port ( D : in STD_LOGIC;
          Res : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC;
          Qbar : out STD_LOGIC);
End component;

    Signal D : STD_LOGIC;
    Signal Res : STD_LOGIC;
    Signal Clk : STD_LOGIC;
    Signal Q : STD_LOGIC;
    Signal Qbar : STD_LOGIC;

begin

UUT: D_FF port map(
    D => D,
    Res => Res,
    Clk => Clk,
    Q => Q,
    Qbar => Qbar);


Clk_process:
process
    begin
        Clk <= '0';
        wait for 50ns;

        Clk <= '1';
        wait for 50ns;

    end process;

process
begin
    D <= '0';      Res <= '1';      wait for 100 ns;
    Res <= '0';    D <= '0';      wait for 100 ns;
    Res <= '0';    D <= '1';      wait for 100 ns;
    Res <= '1';    D <= '1';      wait for 100 ns;
    Res <= '0';    D <= '1';      wait for 100 ns;
    Res <= '1';    D <= '0';      wait for 100 ns;
    Res <= '0';    D <= '0';      wait for 100 ns;
    wait;
end process;
end behavioral;
```

## Timing Diagram

 

## 2) Slow Clock

### Design Source File

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;


entity Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
           Clk_out : out STD_LOGIC);
end Slow_Clk;

architecture Behavioral of Slow_Clk is

    signal count : integer := 1;
    signal clk_status : std_logic := '0';

begin
    process (Clk_in) begin
        if (rising_edge(Clk_in)) then
            count <= count + 1;
            if(count = 5) then
                clk_status <= not clk_status;
                Clk_out <= clk_status;
                count <= 1;
            end if;
        end if;
    end process;
end Behavioral;
```

## Elaborated design schematic

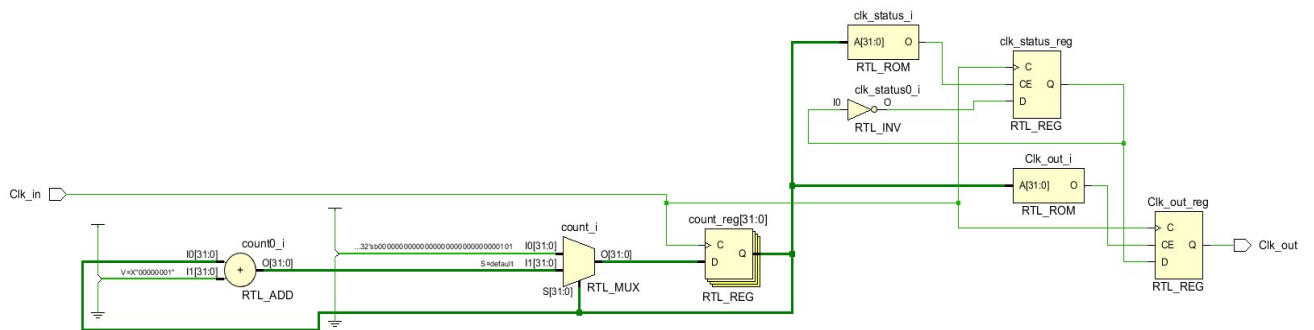

## Simulation File

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Slow_Clk_Sim is
-- Port ( );
end Slow_Clk_Sim;

architecture Behavioral of Slow_Clk_Sim is


signal Clk_in: STD_LOGIC := '0';
signal Clk_out: STD_LOGIC;

begin
-- Instantiate the Unit Under Test (UUT)

UUT:Slow_Clk port map(
    Clk_in => Clk_in,
    Clk_out => Clk_out
);
-- Clock process definitions

Clk_process:
Process
begin
    Clk_in <= '0';
    wait for 10ns;
    Clk_in <= '1';
    wait for 10ns;
end process;
end Behavioral;
```

### Timing Diagram

 

## 3) Counter

### Design Source File

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Counter is
    Port ( Dir : in STD_LOGIC;
          Res : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (2 downto 0));
end Counter;

architecture Behavioral of Counter is

    component D_FF
    port ( D : in STD_LOGIC;
          Res: in STD_LOGIC;
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC;
          Qbar : out STD_LOGIC);
    end component;

    component Slow_Clk
    port ( Clk_in : in STD_LOGIC;
          Clk_out: out STD_LOGIC);
    end component;
```



```

signal D0, D1, D2 : std_logic; -- Internal signals
signal Q0, Q1, Q2 : std_logic; -- Internal signals
signal Clk_Slow   : std_logic; -- Internal clock

begin
Slow_Clk0 : Slow_Clk
port map (
    Clk_in => Clk,
    Clk_out => Clk_slow);

    D0 <= ((not Q2) and (not Dir)) or (Q1 and Dir);
    D1 <= ((not Dir) and Q0) or (Dir and Q2);
    D2 <= ((not Dir) and Q1) or (Dir and (not Q0));

D_FF0 : D_FF
port map (
    D => D0,
    Res => Res,
    Clk => Clk_slow,
    Q => Q0);

D_FF1 : D_FF
port map (
    D => D1,
    Res => Res,
    Clk => Clk_slow,
    Q => Q1);


D_FF2 : D_FF
port map (
    D => D2,
    Res => Res,
    Clk => Clk_slow,
    Q => Q2);

    Q(0) <= Q0;
    Q(1) <= Q1;
    Q(2) <= Q2;

end Behavioral;

```

### Elaborated design schematic

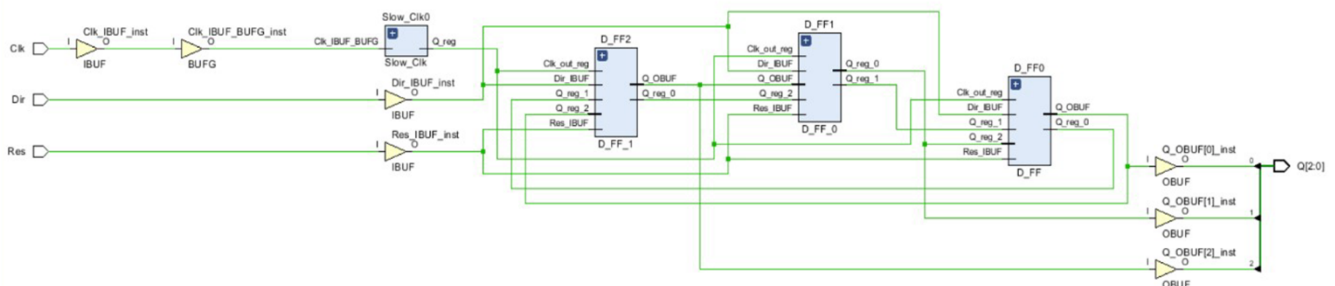

### Simulation File

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Counter_sim is
-- Port ( );
end Counter_sim;

architecture Behavioral of Counter_sim is

    -- Component declarations
    component Counter
        Port ( Dir : in STD_LOGIC;
              Res : in STD_LOGIC;
              Clk : in STD_LOGIC;
              Q : out STD_LOGIC_VECTOR (2 downto 0));
    end component;

    -- Signal declarations
    signal Dir : in STD_LOGIC;
    signal Res : in STD_LOGIC;
    signal Clk : in STD_LOGIC;
    signal Q : out STD_LOGIC_VECTOR (2 downto 0));


begin
    UUT: Counter
        Port map (Dir => Dir,
                  Res => Res,
                  Clk => Clk,
                  Q => Q);

    Clk_process:
    process
    begin
        Clk <= '0';          wait for 10ns;
        Clk <= '1';          wait for 10ns;
    end process;

    process
    begin
        Res <= '1';          Dir <= '0';          wait for 100ns;
        Dir <= '0';          Res <= '0';          wait for 100ns;
        Res <= '0';          wait for 100ns;
        Res <= '1';          Dir <= '1';          wait for 100ns;
        Dir <= '1';          Res <= '0';          wait for 100ns;
        Res <= '1';          wait for 100ns;
        Res <= '0';          Dir <= '1';          wait for 100ns;
        Dir <= '0';          Res <= '0';          wait for 100ns;
        Res <= '1';          wait for 100ns;
        Res <= '0';          Dir <= '1';          wait for 100ns;
        Dir <= '1';          Res <= '1';          wait for 100ns;
        Res <= '0';          wait for 100ns;
        Res <= '0';          Dir <= '0';          wait for 100ns;
        Dir <= '0';
        wait;
    end process;

end Behavioral;
```

### Timing Diagram

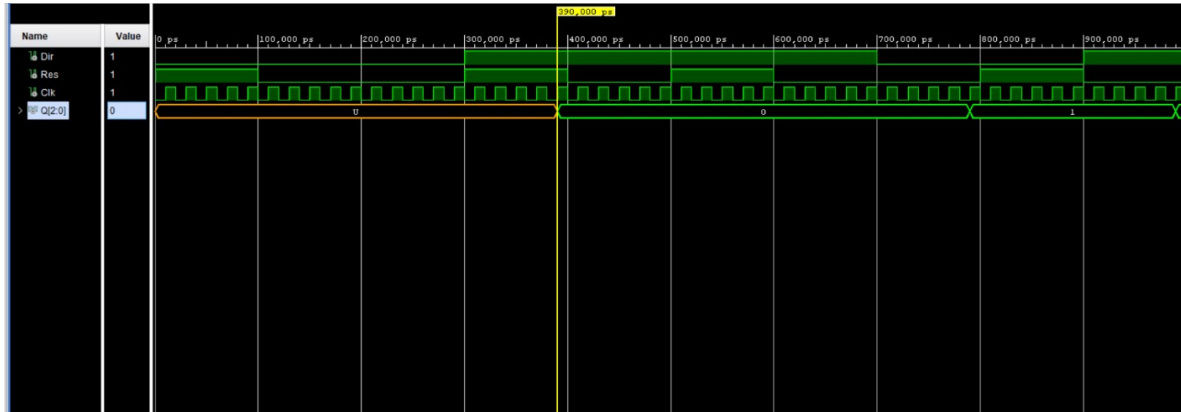

### Constraints File

```
## Clock signal
set_property PACKAGE_PIN W5 [get_ports Clk]
set_property IOSTANDARD LVCMOS33 [get_ports Clk]
create_clock -add -name sys_clk_pin -period 10.00 -waveform
{0 5} [get_ports Clk]

## Switches
set_property PACKAGE_PIN V17 [get_ports {Dir}]
set_property IOSTANDARD LVCMOS33 [get_ports {Dir}]

## LEDs
set_property PACKAGE_PIN U16 [get_ports {Q(0)}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q(0)}]
set_property PACKAGE_PIN E19 [get_ports {Q(1)}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q(1)}]
set_property PACKAGE_PIN U19 [get_ports {Q(2)}]
set_property IOSTANDARD LVCMOS33 [get_ports {Q(2)}]

##Buttons
set_property PACKAGE_PIN U17 [get_ports Res]
set_property IOSTANDARD LVCMOS33 [get_ports Res]
```

### Conclusion

A counter is like a digital gadget that can either increase or decrease its number with each tick of a clock. You can decide if it should count up or down using an external switch. It basically goes through different stages, and each time the clock ticks, the number it shows changes. Depending on what kind of counter it is, you can make it change by giving it a clock tick or using other buttons. People use counters in lots of electronic things to measure time or how often something happens.

-End-